

Figure 2.15 An inverter with the output connected back to the input.