



Figure 2.8 An example of a circuit with three inputs labeled X , Y , and Z . Internal interconnections are also labeled to allow us to discuss intermediate values.