

Lab 2

Digital Logic: Use Of A Breadboard

Purpose

To learn how to wire a basic breadboard and use an LED to test the operation of a gate.

Background Reading And Preparation

Read Chapter 2 to learn about basic logic gates and circuits, and read the beginning sections of this Appendix to learn about breadboards. Attend a lecture on how to properly use the breadboard and related equipment.

Overview

Place a 7400 chip on a breadboard, connect power and ground from a five-volt power supply, connect the inputs of a gate to the four possible combinations of zero and one, and use an LED to observe the output.

Procedure And Details (checkmark as each is completed)

- 1. Obtain a breadboard, power supply, wiring kit, and parts box with the necessary logic gates. Also verify that you have a copy of the textbook or a data sheet that specifies the pins on a 7400 (quad, two-input NAND gate).
- 2. Place the 7400 on the breadboard as Figure A1.2† shows.
- 3. Connect the two wires from a five-volt power supply to two separate sets of sockets near the edge of the board.
- 4. Add a wire jumper that connects pin 14 on the 7400 to five volts.
- 5. Add a wire jumper that connects pin 7 on the 7400 to zero volts. NOTE: be sure not to reverse the connections to the power supply or the chip will be damaged.

.....
†Figure A1.2 can be found on page 334.

- 6. Add a wire jumper that connects pin 1 on the 7400 to zero volts.
- 7. Add a wire jumper that connects pin 2 on the 7400 to zero volts.
- 8. Connect the LED, from the lab kit, between pin 3 on the 7400 and ground (zero volts). NOTE: the LED must be connected with the positive lead attached to the 7400.
- 9. Verify that the LED is lit (it should be lit because both inputs are zero which means the output should be one).
- 10. Move the jumper that connects pin 2 from zero volts to five volts, and verify that the LED remains lit.
- 11. Move the jumper that connects pin 2 back to zero volts, move the jumper that connects pin 3 from zero volts to five volts, and verify that the LED remains lit.
- 12. Keep the jumper from pin 3 on five volts, move the jumper that connects pin 2 to five volts, and verify that the LED goes out.

Optional Extensions (checkmark as each is completed)

- 13. Wire the breadboard as shown in Figure A1.2 (pin 3 connected to pin 12, and pin 13 acting as an additional input).
- 14. Connect the LED between pin 11 and ground.
- 15. Record the LED values for all possible combinations of the three inputs.
- 16. What Boolean function does the circuit represent?