



Figure 2.1 The two types of transistors used in logic circuits. The type labeled (a) turns on when the gate voltage is positive; transistor labeled (b) turns on when the gate voltage is zero (or negative).