



Figure 2.12 A full adder circuit that accepts a carry input as well as two input bits.