



**Figure 2.18** Illustration of a transition diagram that shows how a flip flop reacts to the series of inputs in Figure 2.17. Marks along the x-axis indicate times; each corresponds to one clock tick.