Figure 11.1 Illustration of a miniature static RAM circuit that stores one data bit. The circuit contains multiple transistors.